

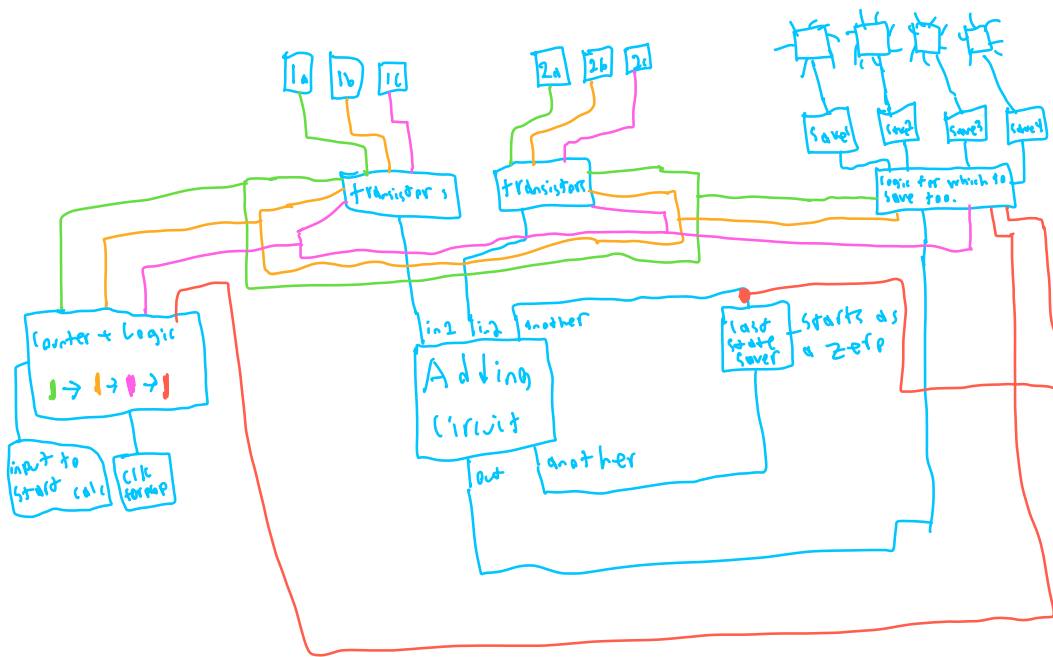


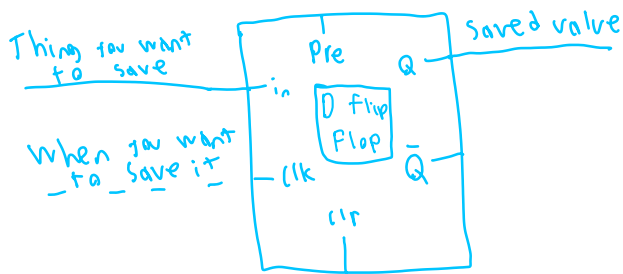

Saving module

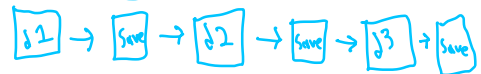

Propagator
↓
counter more efficient



5 bit counter

12 4 8 16 32 64 128 256 512 1024 2048 4096 8192 16384 32768

P	B	C	D	E
0	0	1	1	0

$\overline{A} \overline{B} C D E$
4 gates per bit